



INDIAN INSTITUTE OF INFORMATION TECHNOLOGY UNA [IHP]

An Institute of National Importance under MoE

Saloh, Una (HP) – 177 209

Website: www.iiitu.ac.in

AY 2021- 22


School of Computing




CURRICULUM: IIITUGCSE20

Cycle Test – I

15, Feb.'22

Degree	B. Tech.	Branch	CSE
Semester	I		
Subject Code & Name	EEEC103 (Basic Electrical and Electronics Engineering)		
Time: 60 Minutes	Answer All Questions	Maximum: 20 Marks	

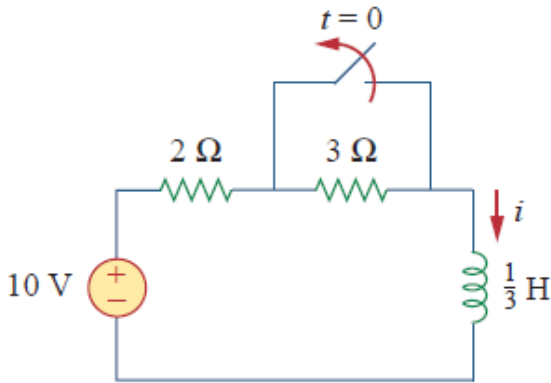Sl. No.	Question	Marks
1.a	Apply the conditions for checking the linearity in an electrical circuit.	(2)
1.b	Construct the variation of XL , XC and R with respect to frequency in parallel resonance.	(2)
2.a	Find $i(t)$ in the circuit of Figure 1 for $t > 0$. Assume that the switch has been closed for a long time.  <p>Figure 1: Circuit diagram for Problem 2. (a)</p>	(2)
2.b	Make use of the balanced Wye-Wye three-phase balanced connection to demonstrate the need of neutral wire from the three-phase source to load.	(2)
3.a	Explain why is it necessary to use a voltage regulator circuit in a power supply.	(1)
3.b	Illustrate the constructional features of a wire-wound resistor.	(1)

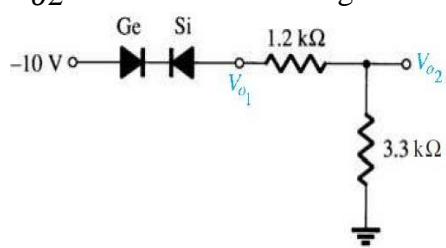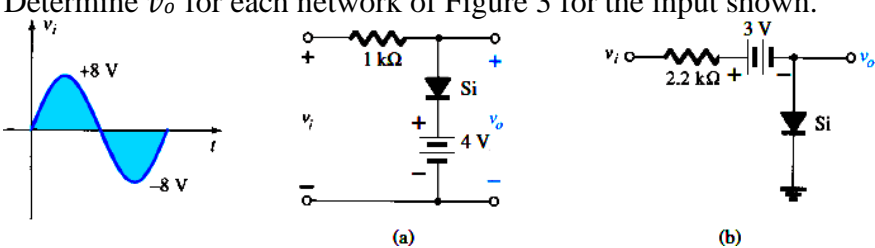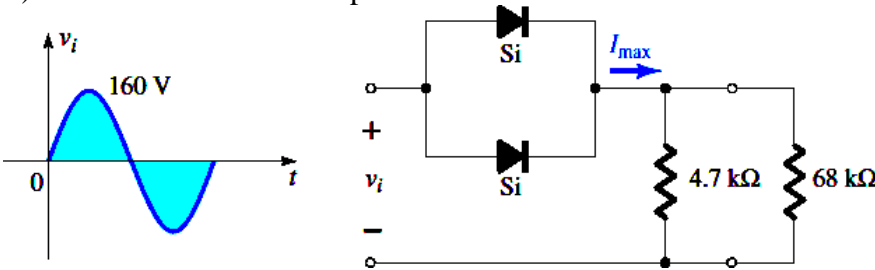3.c	Demonstrate a voltage regulator that will maintain an output voltage of 20 V across a 1-k Ω load with an input that will vary between 30 V and 50 V. That is, determine the proper value of R_S and the maximum current I_{ZM} .	(2)
4.a	<p>Determine V_{O1} and V_{O2} for the network in Figure 2.</p>  <p>Figure 2: Circuit Diagram 4. (a)</p>	(1)
4.b	Discuss the DC load line analysis of a PN junction diode.	(1)
4.c	<p>Determine v_o for each network of Figure 3 for the input shown.</p>  <p>Figure 3: Circuit Diagram for Problem 4. (c)</p>	(2)
5.a	<p>Given $P_{max} = 14 \text{ mW}$ for each diode at Figure 4,</p> <p>i) Determine the maximum current rating of each diode (using the approximate equivalent model).</p> <p>ii) Determine I_{max} for the parallel diodes.</p>  <p>Figure 4: Circuit Diagram for Problem 5. (a)</p>	(2)
5.b	Compare different types of rectifiers on the basis of various comparison parameters. Select the best rectifier for making a voltage regulator power supply with justification	(2)